

Name: Karim Mahmoud Kamal Mohamed







ID: 9203076

Sec: 2


B.N: 10

Work done in the project: I done all the Project alone.

Block Diagram:

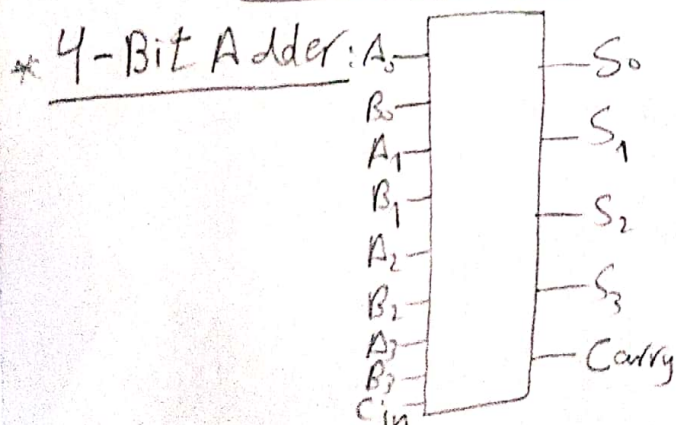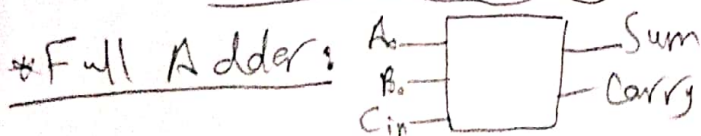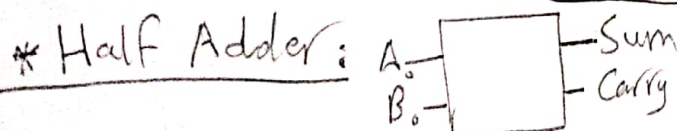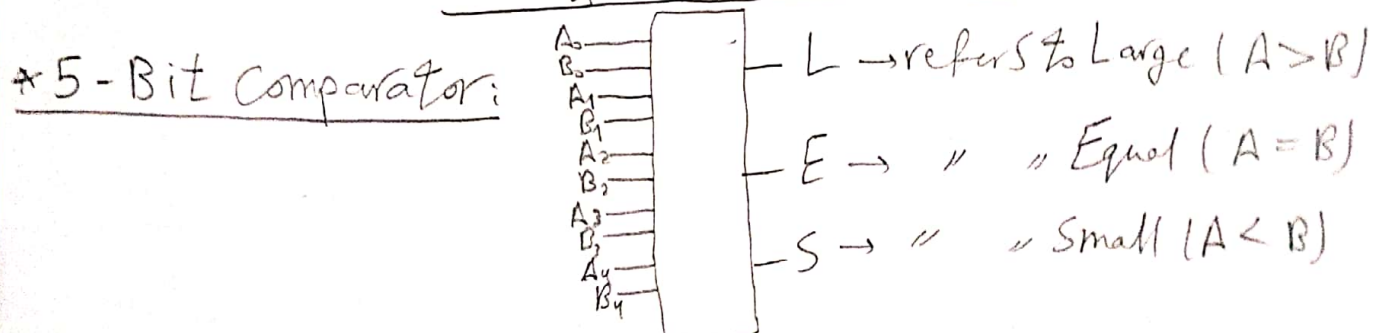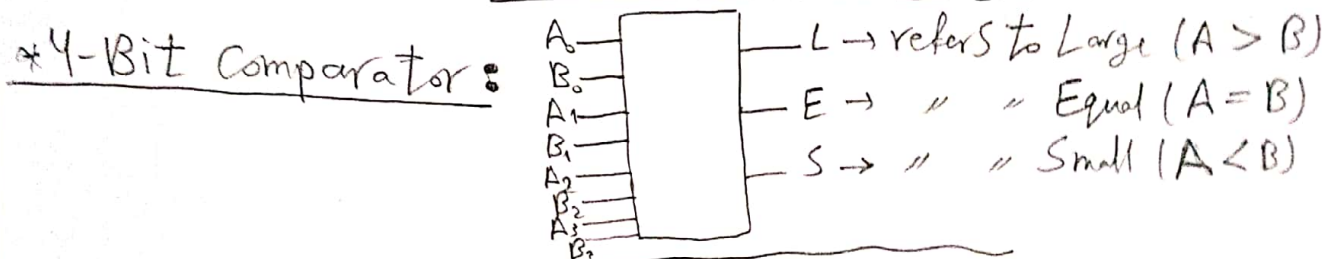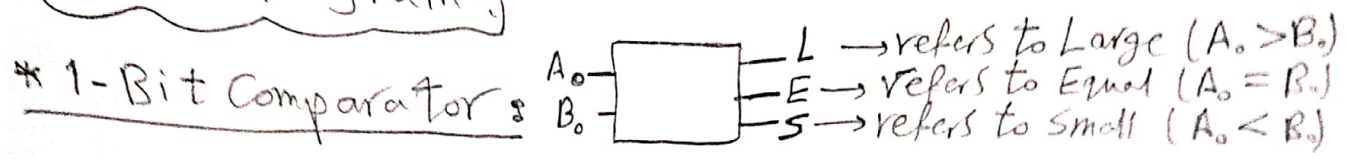

* Final Adder:

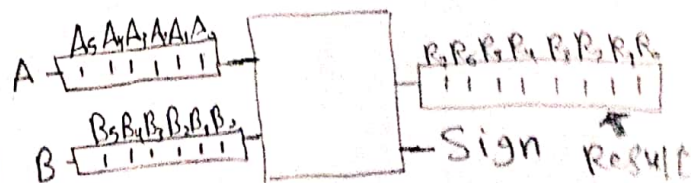


Note: $A_5 \rightarrow$ Sign of A


$B_5 \rightarrow$ Sign of B

$R_5, R_6, R_7 \rightarrow$ always will be Zeros


* Full Subtractor:

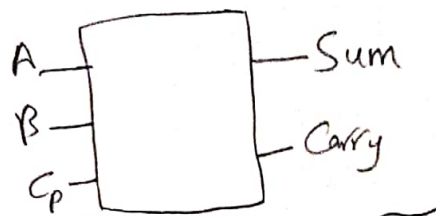

* 4-Bit Subtractor:

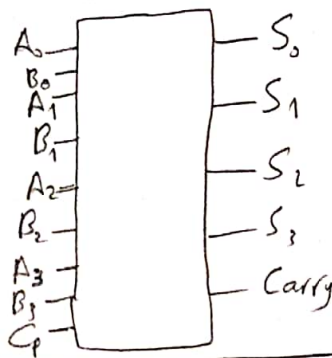


* Final-Subtraction:

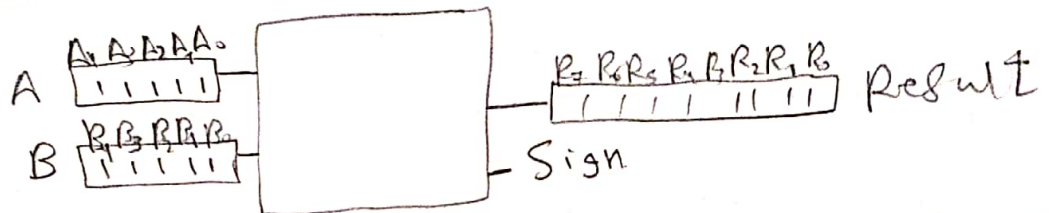


Note: $A_4 \rightarrow$ Sign of A / $B_4 \rightarrow$ Sign of B / $R_4, R_5, R_6, R_7 \rightarrow$ always will be zeros

* Final Multiplication:

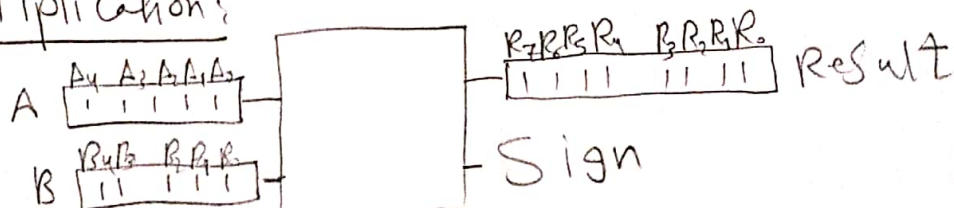


Note: $A_4 \rightarrow$ Sign of A / $B_4 \rightarrow$ Sign of B /

* Final Division:

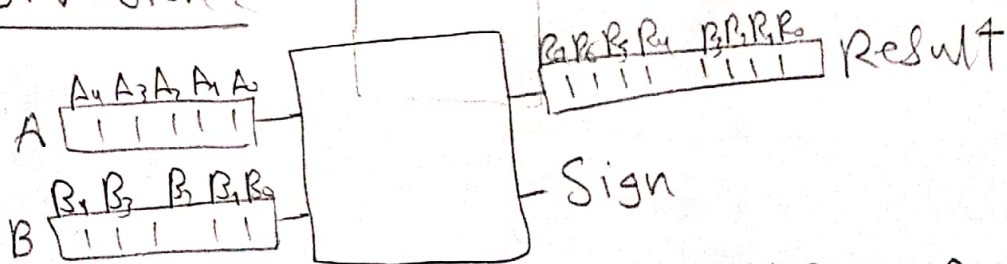


Note: $A_4 \rightarrow$ Sign of A / $B_4 \rightarrow$ Sign of B / $R_4, R_5, R_6, R_7 \rightarrow$ will be always zeros


* Binary To Bcd (4-BITS):

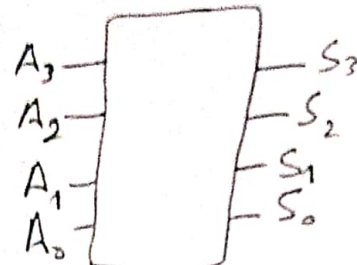

* Binary To Bcd (8-BITS):

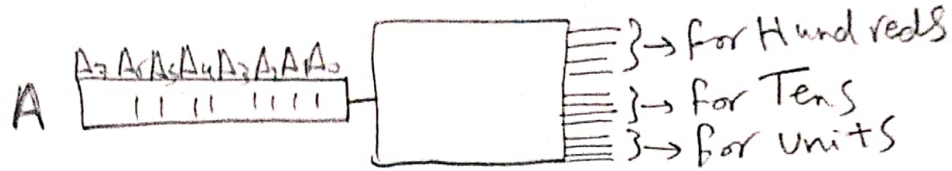


* BCD To 7-Segment:

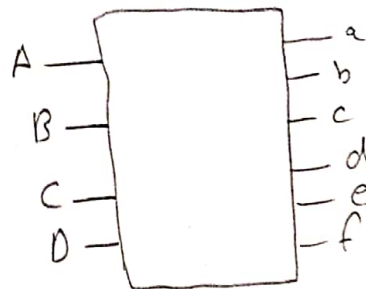


$$\begin{array}{r} a \\ \hline f | \frac{a}{b} \\ e | \frac{c}{d} \end{array}$$

* Full Binary to BCD & 7-Segment:

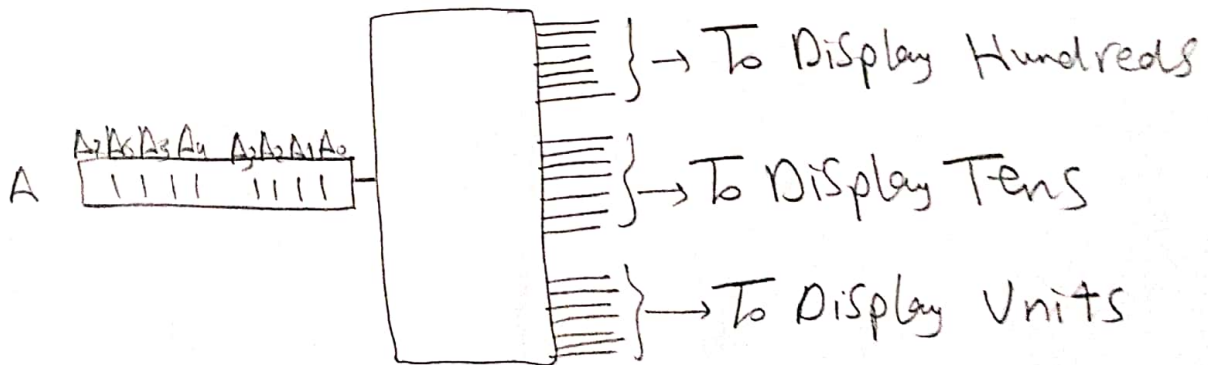

* Main Interface:

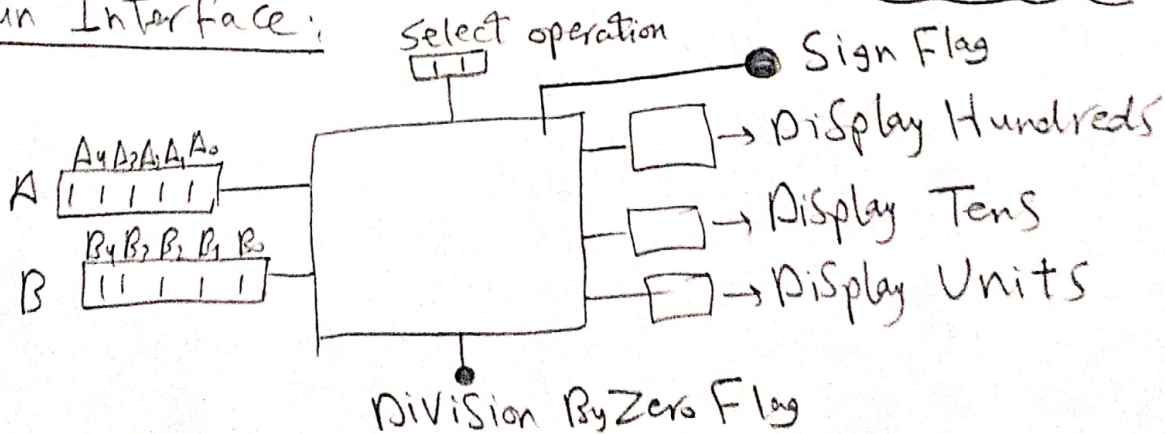

Note: No need for zero Flag as the result zero will be displayed on the 7-Segment Display.

The Coming pages explains
every thing in the project

Important

Select operation

10 → Multiplication

11 → Division

01 → Subtraction

00 → Addition

| A_0 | B_0 | L_0 | S_0 | E_0 |
|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 |

$$L_0 = A_0 B_0'$$

$$S_0 = A_0' B_0$$




$$E_0 = (L_0 + S_0)'$$

$$L = L_3 + E_3 L_2 + E_3 E_2 L_1 + E_3 E_2 E_1 L_0$$


$$S = S_3 + E_3 S_2 + E_3 E_2 S_1 + E_3 E_2 E_1 S_0$$

$$E = E_4 E_3 E_2 E_1 E_0$$

Comparator

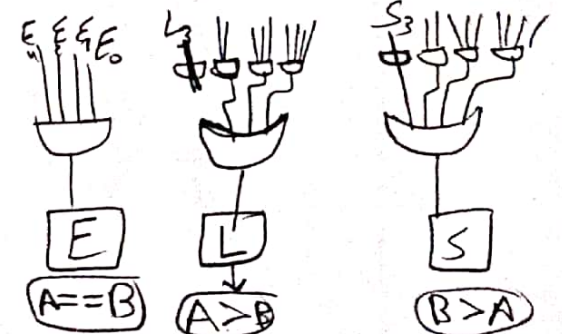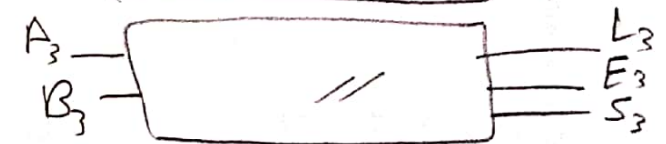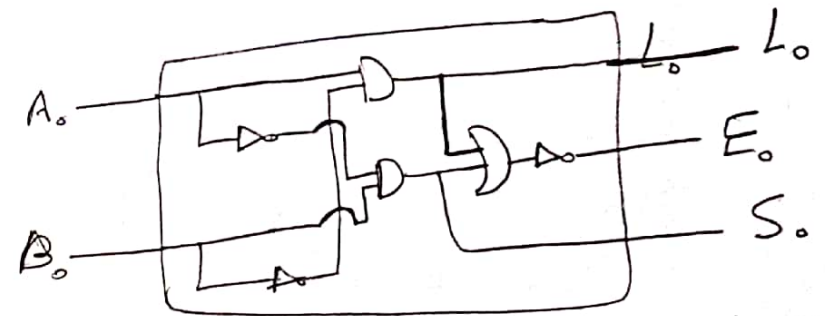

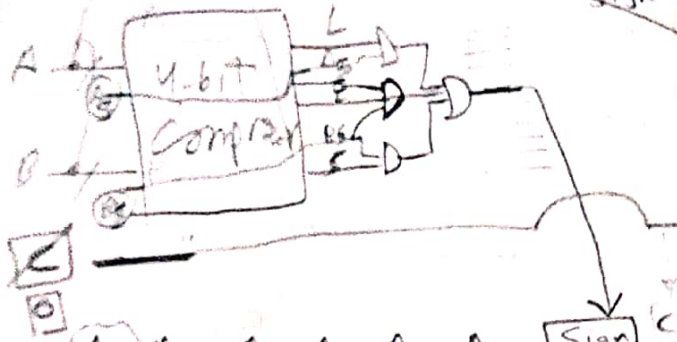Sign $\rightarrow 1$ (-ve) $\rightarrow 0$ (+ve) Addition Circuit



| | | | | | |
|-------|-------|-------|-------|-------|-------|
| A_5 | A_4 | A_3 | A_2 | A_1 | A_0 |
| B_5 | B_4 | B_3 | B_2 | B_1 | B_0 |
| S_5 | S_4 | S_3 | S_2 | S_1 | S_0 |

| | | | | |
|-------|-------|-------|-------|-------|
| A_4 | A_3 | A_2 | A_1 | A_0 |
| B_4 | B_3 | B_2 | B_1 | B_0 |

| | | | | |
|-------|-------|-------|-------|-------|
| S_4 | S_3 | S_2 | S_1 | S_0 |
|-------|-------|-------|-------|-------|

$A > B$

| A_5 | B_5 | Sign |
|-------|-------|------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

$F = A_5$




$B > A$

| A_5 | B_5 | Sign |
|-------|-------|------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |






$F = B_5$

| A | B | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

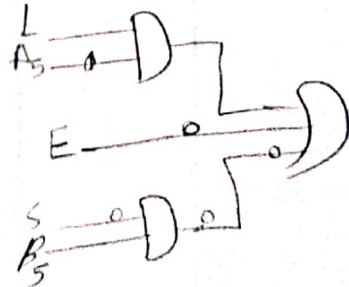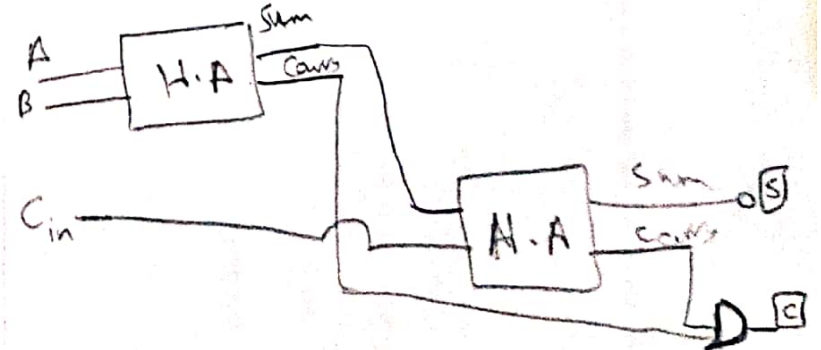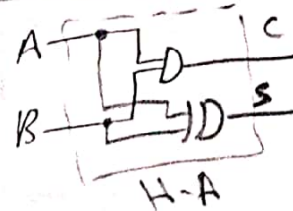$C = AB$
 $S = A'B + AB'$
 $S = A \oplus B$



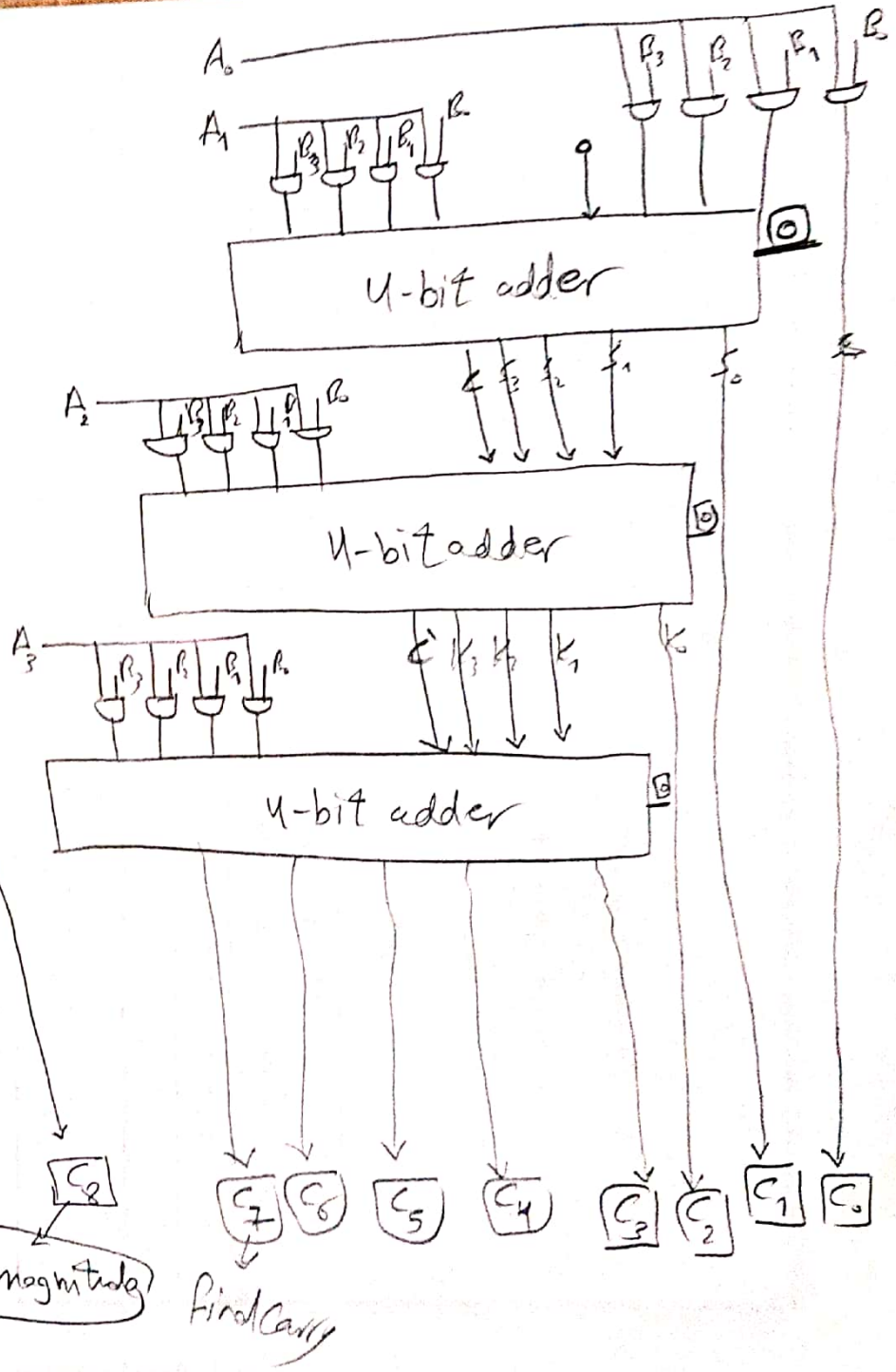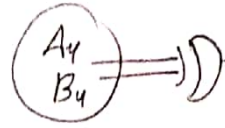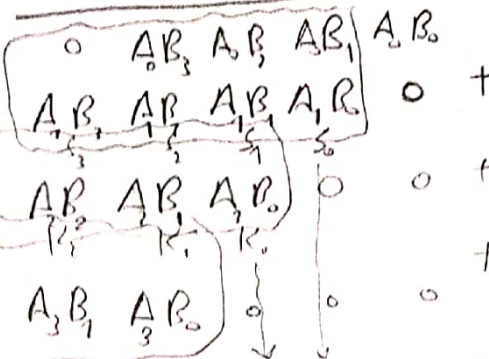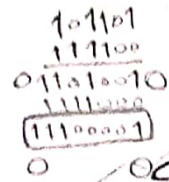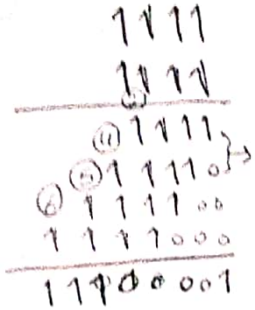$B_3 \quad B_2 \quad B_1 \quad B_0$
 $A_3 \quad A_2 \quad A_1 \quad A_0$



225

| | | |
|---|-----|---|
| 2 | 275 | |
| 2 | 112 | 1 |
| 2 | 56 | 0 |
| 2 | 28 | 0 |
| 2 | 14 | 0 |
| 2 | 7 | 0 |
| 2 | 3 | 1 |
| 2 | 1 | 1 |
| 2 | 0 | 1 |




11100001
Sign magnitude

| A | B | C ₈ |
|---|---|----------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$A \oplus B$

$C_8 = A \odot B$


4- Bit Sub

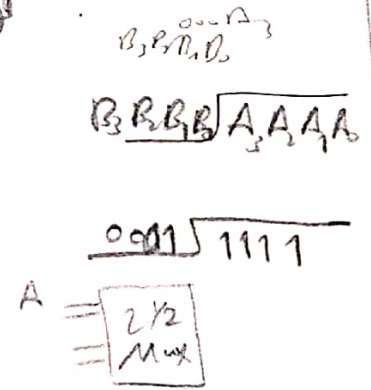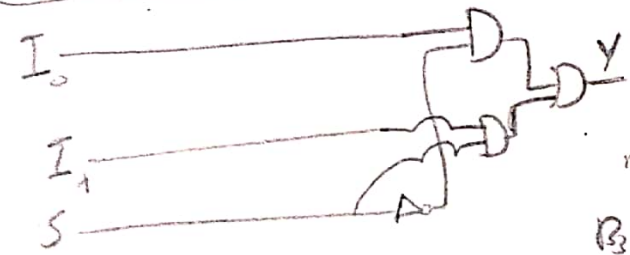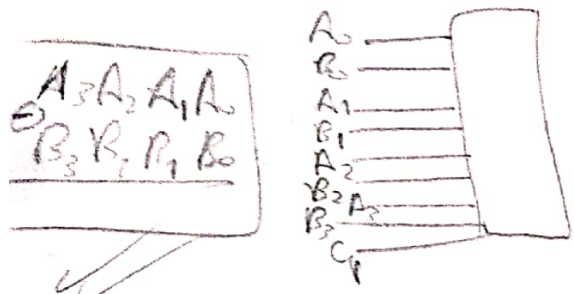

$$\begin{array}{r}
 Q_2 \\
 Q_2 W_3 \\
 V_2 \\
 \hline
 V_2 W_3 \\
 V_2 Q_2 \quad 0 \quad + \\
 \hline
 V_2 Q_2 \quad V_2 W_3
 \end{array}$$

| | | |
|---------------------------|-------------------|---|
| $B_2 B_1 B_0$ | $A_3 A_2 A_1 A_0$ | |
| $A_0 B_2 A_0 B_1 A_0 B_0$ | | |
| $A_1 B_2 A_1 B_1 A_1 B_0$ | 0 | + |
| $A_2 B_2 A_2 B_1 A_2 B_0$ | 0 | 0 |
| $A_3 B_2 A_3 B_1 A_3 B_0$ | C | C |

Division Circuit

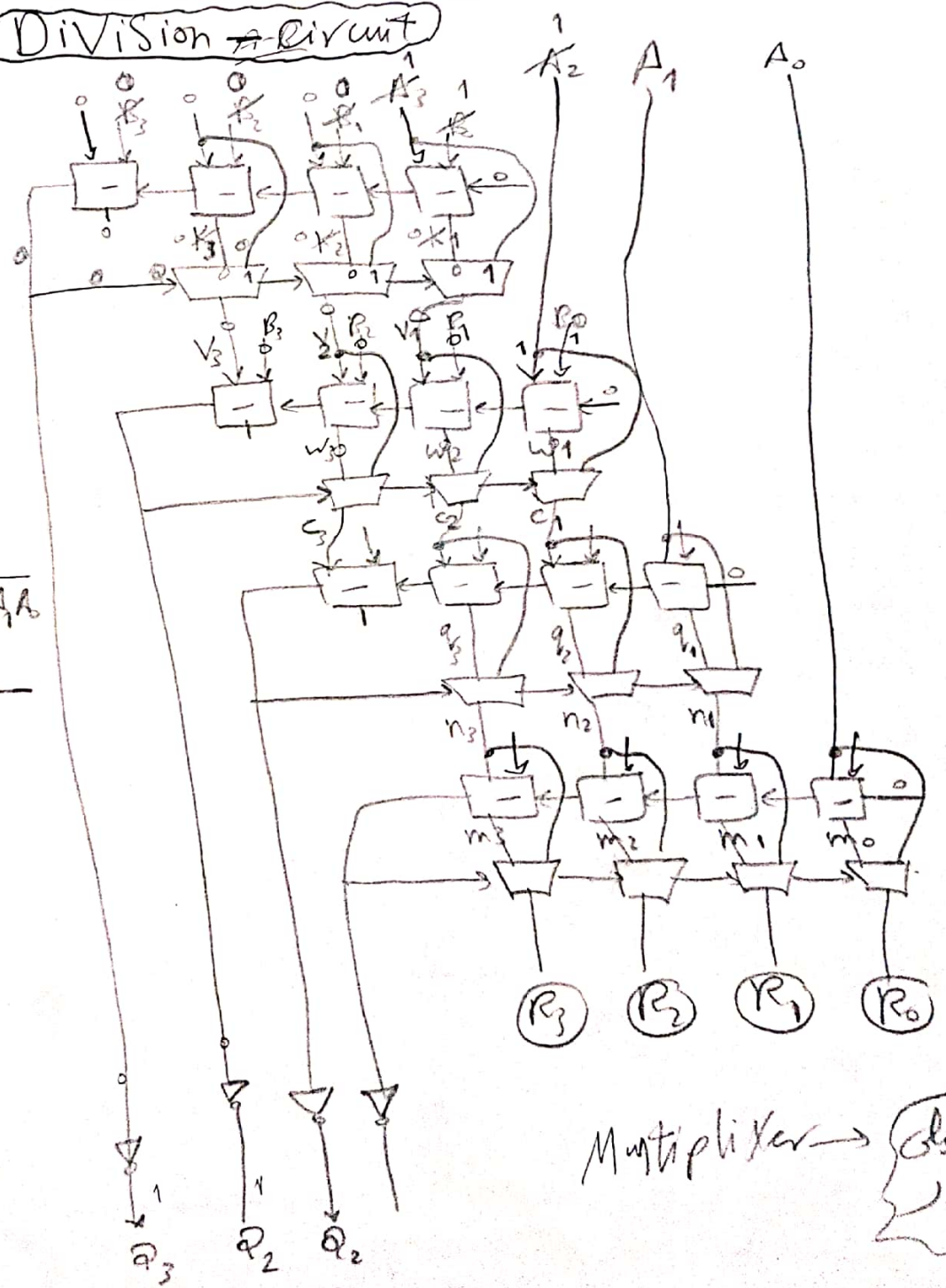

Multiplexer → المتحكم في البيانات

$$\begin{array}{r} 1110 \\ 0011 \\ \hline 10001 \end{array}$$

$$\begin{array}{r} 225 \\ 0111 \\ 0011 \\ \hline 1010 \end{array}$$

$$\begin{array}{r} 0100 \\ 0011 \\ \hline 0111 \end{array}$$

Page/

Date/

$1+7+4+8$
(15)
1111

$$\begin{array}{r} 10 \\ \hline 2 \end{array}$$

$$\begin{array}{r} 1010 \\ \hline 5 \end{array}$$

$$\begin{array}{r} 1111 \end{array}$$

11100001

111 00001

1010 00001

1 0100 0001

1 0111 0001

10 1110 001

101 0001 001

1010 0010 01

1010 0010 01

1 1010 0100 1

1 0101 0111 1

$$\begin{array}{r} 1010 \\ 0011 \\ \hline 1101 \\ 0100 \\ 0011 \\ \hline 0101 \end{array}$$

225

| | A ₃ | A ₂ | A ₁ | A ₀ | S ₃ | S ₂ | S ₁ | S ₀ |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 0 | | | | |
| | 1 | 0 | 1 | 1 | | | | |
| | 1 | 1 | 0 | 0 | | | | |
| | 1 | 1 | 0 | 1 | | | | |
| | 1 | 1 | 1 | 0 | | | | |
| | 1 | 1 | 1 | 1 | | | | |

2

0101

0011

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1000

1111 1111

1+2+4
7

0111








1010

Date/

Page/

A₇ A₆ A₅ A₄ A₃ A₂ A₁ A₀

255

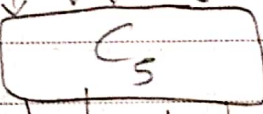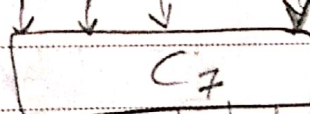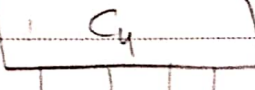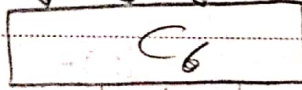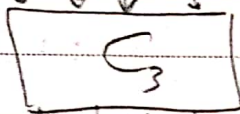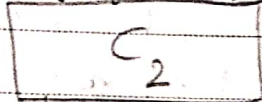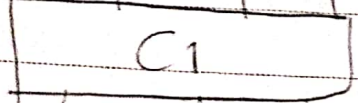

P₈ P₇ P₆ P₅ P₄ P₃ P₂ P₁ P₀

0010 0101 0101

0110 1111

111

0001 0001 0001

A₇
1001 1111

XXXX XXXX

255 8

| | | | | |
|---|---|---|---|---|
| | 0 | 1 | 3 | 2 |
| 4 | 1 | 5 | 1 | 1 |
| X | X | X | X | X |
| 1 | 1 | 1 | X | X |

$$S_3 = A_3 + A_2 A_1 + A_2 A_0$$

| | | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | | 1 | | |
| 01 | X | X | X | X |
| 11 | | 1 | X | X |
| 10 | | | | |

$$S_2 = A_3 A_0 + A_2 \bar{A}_1 \bar{A}_0$$



| | | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | | 1 | 1 | |
| 01 | | 1 | | |
| 11 | X | X | X | X |
| 10 | 1 | | | |

$$S_1 = A_7 A_0 + \bar{A}_2 A_1 + A_3 \bar{A}_0$$


| | | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | | 1 | 1 | |
| 01 | | | | |
| 11 | X | X | X | X |
| 10 | 1 | | | |

$$S_0 = A_3 \bar{A}_0 + \bar{A}_3 \bar{A}_2 \bar{A}_0 + A_2 A_1 A_0$$


| | | | | | | | |
|---|---|---|---|---|---|---|---|
| A | B | C | D | E | F | G | H |
|---|---|---|---|---|---|---|---|

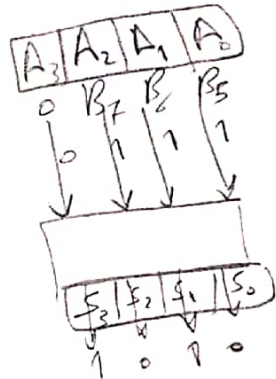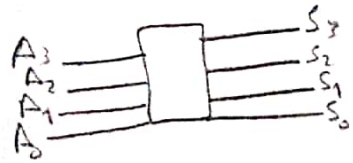

Binary To BCD (8-Bits)

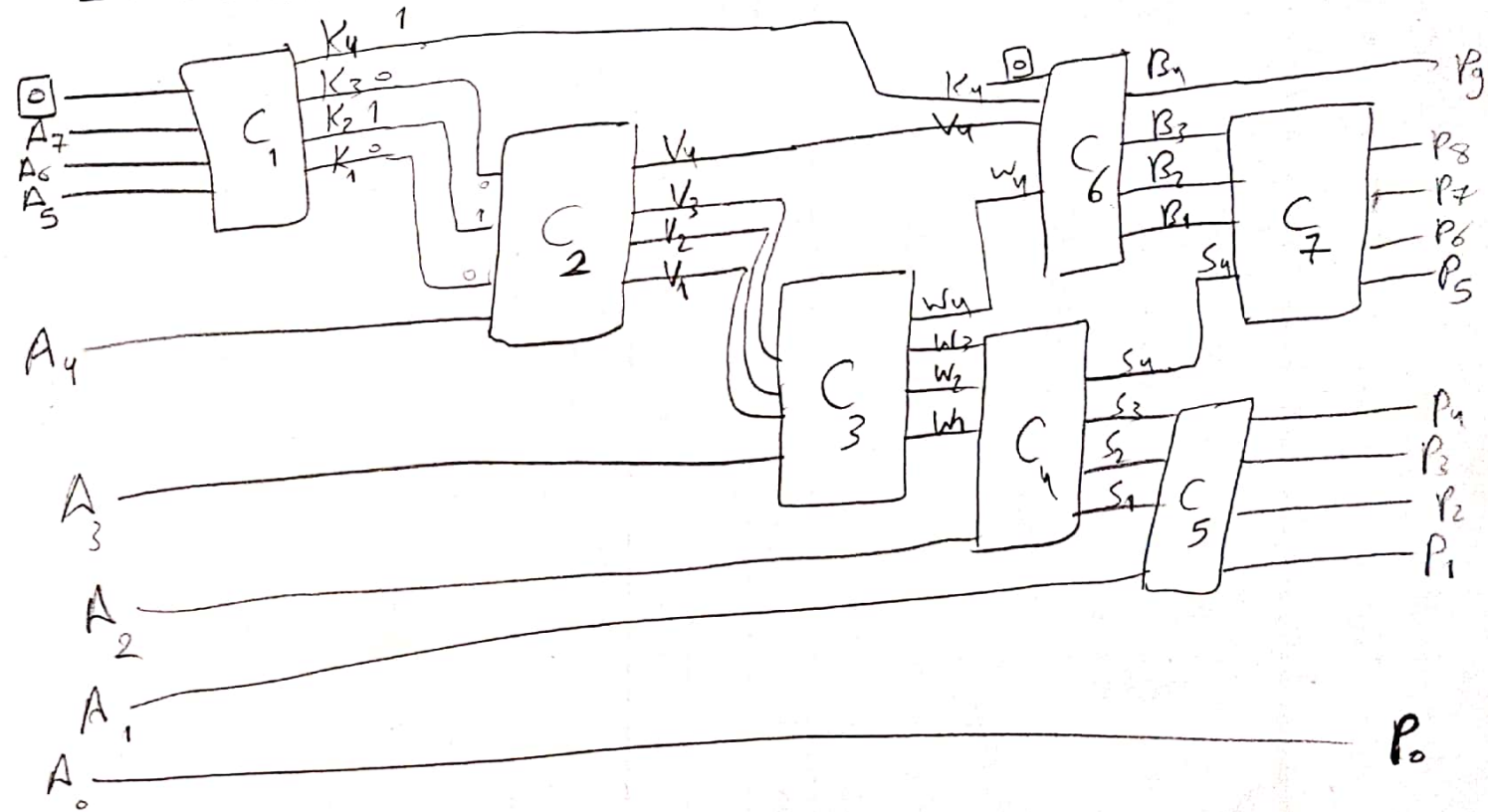
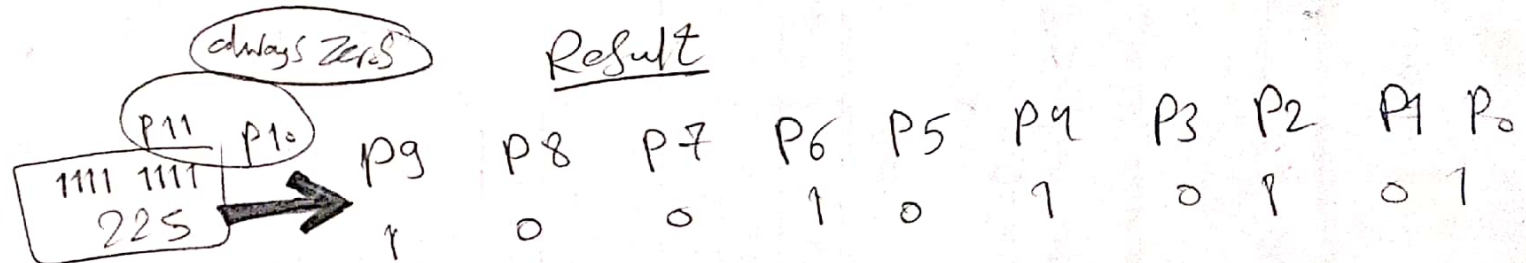
$$\begin{aligned}
 S_3 &= A_3 + A_2 A_1 + A_2 A_0 \\
 S_2 &= A_3 A_0 + A_2 \bar{A}_1 \bar{A}_0 \\
 S_1 &= A_1 A_0 + A_1 \bar{A}_2 + A_1 \bar{A}_3 \\
 S_0 &= A_3 \bar{A}_0 + \bar{A}_3 \bar{A}_2 A_0 + A_2 A_1 \bar{A}_0
 \end{aligned}$$



* BCD to Seven-Segment Decoder *

| | A | B | C | D | a | b | c | d | e | f | g |
|----|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 10 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 11 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 12 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 14 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 15 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

* we can not use the don't care condition here for the six binary combinations 10101-1111, as the design will most likely produce some arbitrary and meaningless display of the unused combinations

$$a = \bar{A}C + \bar{A}BD + \bar{B}C\bar{D} + A\bar{B}\bar{C}$$

$$b = \bar{A}\bar{B} + \bar{A}C\bar{D} + \bar{A}C\bar{D} + A\bar{B}\bar{C}$$

$$c = \bar{A}\bar{B} + \bar{A}D + \bar{B}C\bar{D} + A\bar{B}\bar{C}$$

$$d = \bar{A}C\bar{D} + \bar{A}\bar{B}C + \bar{B}C\bar{D} + A\bar{B}C + A\bar{B}\bar{C}$$


$$e = \bar{A}C\bar{D} + \bar{B}C\bar{D}$$

$$f = \bar{A}\bar{B}\bar{C} + \bar{A}C\bar{D} + \bar{A}B\bar{D} + A\bar{B}\bar{C}$$

$$g = \bar{A}C\bar{D} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

14 AND gate

7 OR gate

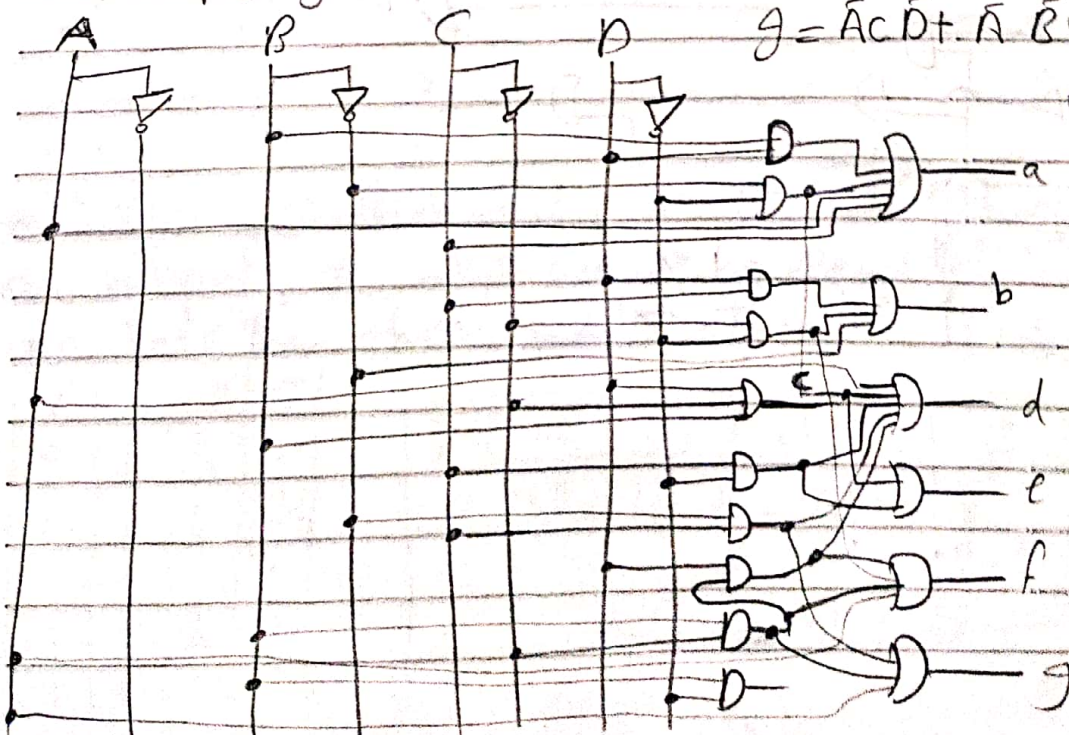

$$a = A + C + \bar{B}\bar{D} + \bar{B}\bar{D}$$

$$a = \bar{A}C + \bar{A}BD + \bar{B}C\bar{D} + A\bar{B}\bar{C}$$

| | A | B | C | D | a | b | c | d | e | f | g |
|---|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |

| | | | |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 1 | | 1 | 1 |
| | 1 | 1 | 1 |
| x | x | x | x |
| 1 | 1 | x | x |

$$a = A + C + \bar{B}\bar{D} + BD$$

| | | | |
|---|---|---|---|
| 1 | 1 | 1 | |
| 1 | 1 | 1 | 1 |
| x | x | x | x |
| 1 | 1 | x | x |

$$c = \bar{C} + D + B$$

| | | | |
|---|---|---|---|
| 1 | | | 1 |
| | | | 1 |
| x | x | x | x |
| 1 | | x | x |

$$e = c\bar{D} + \bar{B}\bar{D}$$

| | | | |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 1 | 1 | 1 | 1 |
| 1 | x | 1 | x |
| x | x | x | x |
| 1 | 1 | x | x |

$$b = A + \bar{B} + \bar{C}\bar{D} + CD$$

| | | | |
|---|---|---|---|
| 1 | 0 | 1 | 1 |
| | 1 | | 1 |
| x | x | x | x |
| 1 | 1 | x | x |

$$d = A + \bar{B}\bar{D} + c\bar{D} + \bar{B}c + B\bar{C}D$$

| | | | |
|---|---|---|---|
| 1 | | | 1 |
| 1 | 1 | | x |
| x | x | x | x |
| 1 | 1 | x | x |

$$f = \bar{C}\bar{D} + A\bar{C} + B\bar{C} + B\bar{D}$$

| | | | |
|---|---|---|---|
| | | 1 | 1 |
| 1 | 1 | | 1 |
| x | x | x | x |
| 1 | 1 | x | x |

$$g = c\bar{D} + \bar{B}c + B\bar{C} + A\bar{C}$$

$$\begin{aligned}
 a &= A + C + \bar{B}\bar{D} + BD \\
 b &= A + \bar{B} + \bar{C}\bar{D} + CD \\
 c &= \bar{C} + D + B \\
 d &= A + \bar{B}\bar{D} + c\bar{D} + \bar{B}c + B\bar{C}D \\
 e &= c\bar{D} + \bar{B}\bar{D} \\
 f &= \bar{C}\bar{D} + A\bar{C} + B\bar{C} + B\bar{D} \\
 g &= c\bar{D} + \bar{B}c + B\bar{C} + A\bar{C}
 \end{aligned}$$

7-Segment